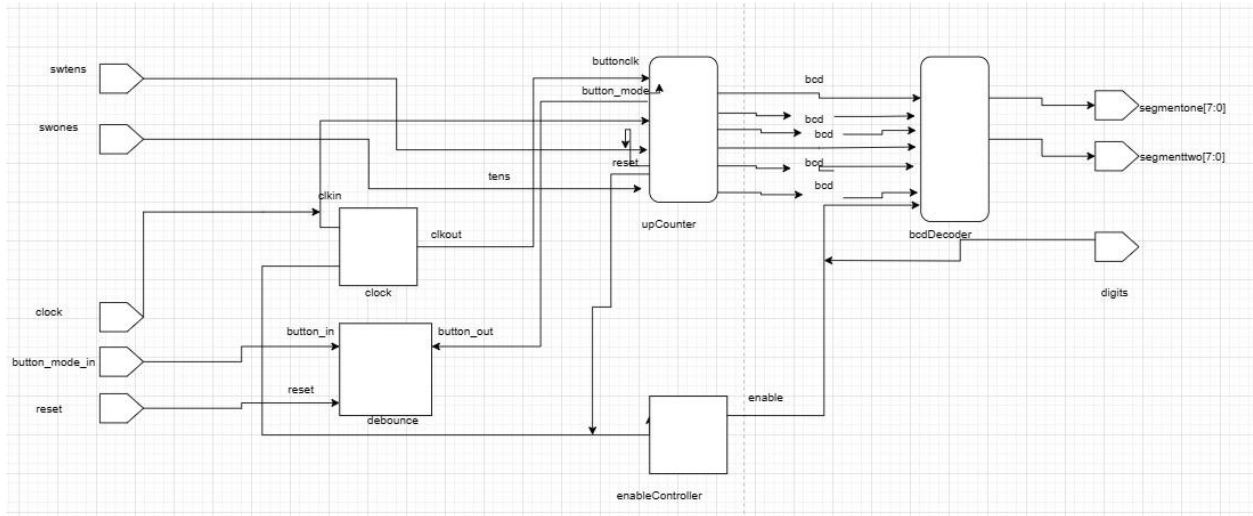


1. **Topic:** Finite State Machine (FSM)

2. **Design structure:**



3. **Code:**

```
module clock_24h_set(clk, B, rst, Y, Z, scan, dec, unit);
    input clk, rst, B;
    input [3:0] dec, unit;
    output [7:0] Y, Z;
    output reg [5:0] scan;
    wire clk_fast_out, clk_1hz_out;
    wire [3:0] bcd1, bcd2, bcd3, bcd4, bcd5, bcd6;
    integer x, a, b;
    reg [3:0] bcd_out;
    wire ctrl_button;

    d_bounce(clk, rst, B, ctrl_button);
    clk_fast(clk, rst, clk_fast_out);
    clk_divider_1hz(clk, rst, clk_1hz_out);

    integer state;
    integer idle = 0;
    integer sec = 1;
    integer min = 2;
    integer hr = 3;
```

```

always@(posedge clk_1hz_out or posedge rst)begin
    if(rst) state<=idle;
    else begin
        case(state)
            idle:begin
                if(ctrl_button)state<=sec;
                else state<=idle;
            end
            sec:begin
                if(ctrl_button)state<=min;
                else state<=sec;
            end
            min:begin
                if(ctrl_button)state<=hr;
                else state<=min;
            end
            hr:begin
                if(ctrl_button)state<=idle;
                else state<=hr;
            end
        endcase
    end
end

counters(clk_1hz_out, rst, bcd1, bcd2, bcd3, bcd4, bcd5, bcd6, state,
dec, unit);
always @(posedge clk_fast_out or posedge rst)begin
    if(rst)
        x<=0;
    else if (x==5) begin
        x<=0;
    end
    else
        x<=x+1;
end
always @(posedge clk_fast_out)begin
    case(x)
        0:begin
            bcd_out<=bcd1;
            scan<=6'b000001;
        end
        1:begin
            bcd_out<=bcd2;

```

```
        scan<=6'b000010;
    end
    2:begin
        bcd_out<=bcd3;
        scan<=6'b000100;
    end
    3:begin
        bcd_out<=bcd4;
        scan<=6'b001000;
    end
    4:begin
        bcd_out<=bcd5;
        scan<=6'b010000;
    end
    5:begin
        bcd_out<=bcd6;
        scan<=6'b100000;
    end
endcase
end
bcd_to_7seg1(bcd_out, Y);
bcd_to_7seg2(bcd_out, Z);
endmodule
```

```
module clk_divider_1hz(clk,rst, clk_out);
    input clk, rst;
    output reg clk_out;
    integer cnt;
    always @(posedge clk or posedge rst) begin
        if (rst)
            cnt<=0;
        else if (cnt==100000000)
            cnt<=0;
        else
            cnt<=cnt+1;
    end
    always @(posedge clk or posedge rst) begin
        if (rst)
            clk_out<=0;
        else if (cnt<=50000000)
            clk_out<=1'b1;
    end
endmodule
```

```

        else
            clk_out<=1'b0;
        end
    endmodule

module clk_btn(clk, rst, clk_out);
    input clk, rst;
    output reg clk_out;
    integer cnt;
    always @(posedge clk or posedge rst) begin
        if (rst)
            cnt<=0;
        else if (cnt==1000000)
            cnt<=0;
        else
            cnt<=cnt+1;
    end
    always @(posedge clk or posedge rst) begin
        if (rst)
            clk_out<=0;
        else if (cnt<=500000)
            clk_out<=1'b1;
        else
            clk_out<=1'b0;
    end
endmodule

module clk_fast(clk, rst, clk_out);
    input clk, rst;
    output reg clk_out;
    integer cnt;
    always@(posedge clk or posedge rst)
    begin
        if(rst) cnt <=0;
        else if(cnt==100000)
            cnt<=0;
        else
            cnt<=cnt+1;
    end
    always @ (posedge(clk) or posedge rst)
    begin
        if (rst) clk_out <= 0;
        else if(cnt<=50000)clk_out<=1'b1;
    end
endmodule

```

```
        else clk_out<=1'b0;
    end
endmodule
```

```
module clk_slow(clk, rst, clk_out);
    input clk, rst;
    output reg clk_out;
    integer cnt;
    always@(posedge clk or posedge rst)
    begin
        if(rst) cnt <=0;
        else if(cnt==1000000)
            cnt<=0;
        else
            cnt<=cnt+1;
        end
    always @ (posedge(clk) or posedge rst)
    begin
        if (rst) clk_out <= 0;
        else if(cnt<=500000)clk_out<=1'b1;
        else clk_out<=1'b0;
    end
endmodule

module and_gate(x, y, f);
    input x, y;
    output f;
    assign f = x & y;
endmodule

module dff(clk, rst, D, Q);
    input clk, rst, D;
    output reg Q;
    always @(posedge (clk) or posedge rst) begin
        if (rst) Q <= 1'b0;
        else Q <= D;
    end
endmodule

module d_bounce(clk, rst, D, d_bnc);
    input clk, rst, D;
    output d_bnc;
    wire [2:0] Q;
    wire clk_div, 1;
```

```
    clk_fast u1(clk, rst, clk_div);
    dff d1(clk_div, rst, D, Q[0]);
    dff d2(clk_div, rst, Q[0], Q[1]);
    dff d3(clk_div, rst, Q[1], Q[2]);
    and_gate and1(Q[0], Q[1], 1);
    and_gate and2(Q[2], 1, d_bnc);
endmodule

module counters(clk, rst, bcd1, bcd2, bcd3, bcd4, bcd5, bcd6, state, dec,
unit);
    input clk, rst;
    input [3:0]dec, unit;
    input [31:0] state;
    output reg [3:0] bcd1, bcd2, bcd3, bcd4, bcd5, bcd6;
    integer cnt1, cnt2, cnt3, cnt4, cnt5, cnt6;
    integer a, b;

    always@(posedge clk or posedge rst)begin
        if(rst)begin
            a<=0;
            b<=0;
        end
        else begin
            case(unit)
                4'b0001: a = 1;
                4'b0010: a = 2;
                4'b0011: a = 3;
                4'b0100: a = 4;
                4'b0101: a = 5;
                4'b0110: a = 6;
                4'b0111: a = 7;
                4'b1000: a = 8;
                4'b1001: a = 9;
                4'b1010: a = 9;
                4'b1011: a = 9;
                4'b1100: a = 9;
                4'b1101: a = 9;
                4'b1110: a = 9;
                4'b1111: a = 9;
                default: a = 0;
            endcase
            case(dec)
                4'b0001: b = 1;
```

```
        4'b0010: b = 2;
        4'b0011: b = 3;
        4'b0100: b = 4;
        4'b0101: b = 5;
        4'b0110: b = 6;
        4'b0111: b = 7;
        4'b1000: b = 8;
        4'b1001: b = 9;
        4'b1010: b = 9;
        4'b1011: b = 9;
        4'b1100: b = 9;
        4'b1101: b = 9;
        4'b1110: b = 9;
        4'b1111: b = 9;
        default: b = 0;
    endcase
end
end
always@(posedge clk or posedge rst) begin //cnt1
    if(rst) begin
        cnt1<=0;
        cnt2<=0;
        cnt3<=0;
        cnt4<=0;
        cnt5<=0;
        cnt6<=0;
    end
    else
        case(state)
            0:begin
                cnt1<=cnt1+1;
                if(cnt1>=9)begin
                    cnt1<=0;
                    cnt2<=cnt2+1;
                    if(cnt2>=5)begin
                        cnt2<=0;
                        cnt3<=cnt3+1;
                        if(cnt3>=9)begin
                            cnt3<=0;
                            cnt4<=cnt4+1;
                            if(cnt4>=5)begin
                                cnt4<=0;
                                cnt5<=cnt5+1;
```

```
        if(cnt5>=9)begin
            cnt5<=0;
            cnt6<=cnt6+1;
        end
        else if(cnt5>=3 && cnt6>=2)begin
            cnt5<=0;
            cnt6<=0;
        end
    end
end
end
end
1:begin
    cnt1<=a;
    cnt2<=b;
    if(a > 9)begin
        cnt1<=9;
    end
    if(b > 5)begin
        cnt1<=9;
        cnt2<=5;
    end
end
end
2:begin
    cnt3<=a;
    cnt4<=b;
    if(a > 9)begin
        cnt3<=9;
    end
    if(b > 5)begin
        cnt3 <=9;
        cnt4<=5;
    end
end
end
3:begin
    cnt5<=a;
    cnt6<=b;
    if(b < 2 & a > 9)begin
        cnt5<=9;
    end
    else if(b >= 2 & a >= 3)begin
        cnt5<=3;
    end
end
end
```



```
        end
        if(b > 2)begin
            cnt5<=3;
            cnt6<=2;
        end
    end
endcase
end
always @(cnt1) begin
    case(cnt1)
        1      : bcd1 = {4'b0001};
        2      : bcd1 = {4'b0010};
        3      : bcd1 = {4'b0011};
        4      : bcd1 = {4'b0100};
        5      : bcd1 = {4'b0101};
        6      : bcd1 = {4'b0110};
        7      : bcd1 = {4'b0111};
        8      : bcd1 = {4'b1000};
        9      : bcd1 = {4'b1001};
        default: bcd1 = {4'b0000};
    endcase
end
always @(cnt2) begin
    case(cnt2)
        1      : bcd2 = {32'b0001};
        2      : bcd2 = {32'b0010};
        3      : bcd2 = {32'b0011};
        4      : bcd2 = {32'b0100};
        5      : bcd2 = {32'b0101};
        default: bcd2 = {32'b0000};
    endcase
end
always @(cnt3) begin
    case(cnt3)
        1      : bcd3 = {4'b0001};
        2      : bcd3 = {4'b0010};
        3      : bcd3 = {4'b0011};
        4      : bcd3 = {4'b0100};
        5      : bcd3 = {4'b0101};
        6      : bcd3 = {4'b0110};
        7      : bcd3 = {4'b0111};
        8      : bcd3 = {4'b1000};
        9      : bcd3 = {4'b1001};
```

```

        default: bcd3 = {4'b0000};
    endcase
end
always @(cnt4) begin
    case(cnt4)
        1      : bcd4 = {4'b0001};
        2      : bcd4 = {4'b0010};
        3      : bcd4 = {4'b0011};
        4      : bcd4 = {4'b0100};
        5      : bcd4 = {4'b0101};
        default: bcd4 = {4'b0000};
    endcase
end
always @(cnt5) begin
    case(cnt5)
        1      : bcd5 = {4'b0001};
        2      : bcd5 = {4'b0010};
        3      : bcd5 = {4'b0011};
        4      : bcd5 = {4'b0100};
        5      : bcd5 = {4'b0101};
        6      : bcd5 = {4'b0110};
        7      : bcd5 = {4'b0111};
        8      : bcd5 = {4'b1000};
        9      : bcd5 = {4'b1001};
        default: bcd5 = {4'b0000};
    endcase
end
always @(cnt6) begin
    case(cnt6)
        1      : bcd6 = {4'b0001};
        2      : bcd6 = {4'b0010};
        default: bcd6 = {4'b0000};
    endcase
end
endmodule

module bcd_to_7seg1(bcd_in, Y);
    input [3:0] bcd_in;
    output reg [7:0] Y;
    always @(bcd_in) begin
        case({bcd_in})
            4'b0001 : Y = {8'b01100000};
            4'b0010 : Y = {8'b11011010};
            4'b0011 : Y = {8'b11110010};
        endcase
    end
end

```

```

        4'b0100 : Y = {8'b01100110};
        4'b0101 : Y = {8'b10110110};
        4'b0110 : Y = {8'b10111110};
        4'b0111 : Y = {8'b11100000};
        4'b1000 : Y = {8'b11111110};
        4'b1001 : Y = {8'b11110110};
        4'b1010 : Y = {8'b11101110};
        4'b1011 : Y = {8'b00111110};
        4'b1100 : Y = {8'b10011100};
        4'b1101 : Y = {8'b01111010};
        4'b1110 : Y = {8'b10011110};
        4'b1111 : Y = {8'b10001110};
        default: Y = {8'b11111100};
    endcase
end
endmodule



module bcd_to_7seg2(bcd_in, Z);
    input [3:0] bcd_in;
    output reg [7:0] Z;
    always @(bcd_in) begin
        case({bcd_in})
            4'b0001 : Z = {8'b01100000};
            4'b0010 : Z = {8'b11011010};
            4'b0011 : Z = {8'b11110010};
            4'b0100 : Z = {8'b01100110};
            4'b0101 : Z = {8'b10110110};
            4'b0110 : Z = {8'b10111110};
            4'b0111 : Z = {8'b11100000};
            4'b1000 : Z = {8'b11111110};
            4'b1001 : Z = {8'b11110110};
            4'b1010 : Z = {8'b11101110};
            4'b1011 : Z = {8'b00111110};
            4'b1100 : Z = {8'b10011100};
            4'b1101 : Z = {8'b01111010};
            4'b1110 : Z = {8'b10011110};
            4'b1111 : Z = {8'b10001110};
            default: Z = {8'b11111100};
        endcase
    end
endmodule

```
  
#### 4. Result:



Normal Counter

When the 8 on the left side is high. The display is set to 59. Then I pressed set and saved the state.



Set next state to 11 and save state

 
 
The maximum value of the last display is 23



When the set button is pressed start to count

Reset is pressed so start to count again

from desired position

  

##### 5. Reflection:

It was funny to work with the constraints because we needed to refine the code and follow the guidelines accurately.